

## Use of 3RB22, 3RB23 and 3RB24 solid-state overload relays up to 820 A with external 3UF18 current transformer (intermediate transformer)

### Description

The 3RB22, 3RB23 and 3RB24 solid-state overload relays can also be used to protect loads up to 820 A by means of an external current transformer. The secondary lines of the current transformer are looped through the three through holes of the current measuring module and are then short-circuited. The secondary current of the external current transformer is the primary current of the current measuring module (3RB29) of the 3RB22, 3RB23 or 3RB24 solid-state overload relay.

### Caution

If nominal current flows through the main circuit, the secondary current of the current transformer must lie within the setting range of the employed current measuring module!

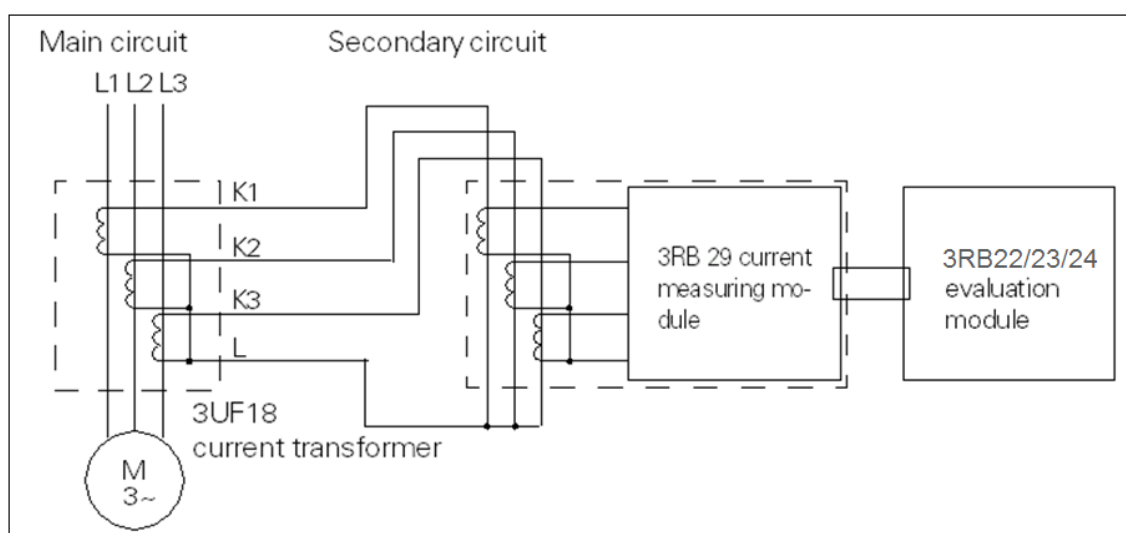


Fig. 1: Current measuring with external 3UF18 current transformer

### Ratio (general)

The ratio can be calculated on the basis of the following formula:

$$\text{Ratio} = \frac{\text{Primary current (external current transformer)}}{\text{Secondary current (external current transformer)}}$$

### Technical data of the current transformer (if not 3UF18)

- Secondary current: 1 A
- Frequency: 50 Hz/60 Hz
- Transformer capacity: Recommended  $\geq 2.5$  VA, depending on secondary current and line length
- Overcurrent factor: 5P10 or 10P10
- Accuracy class: 1

**Example 1:**

- 3UF1868-3GA00 current transformer:
  - Primary current: 820 A with nominal load
  - Secondary current: 1 A
- 3RB22, 3RB23 or 3RB24 solid-state overload relay with 3RB2906-2BG1 current measuring module, setting current 0.3 A to 3 A

**i.e.:**

- The secondary current of the current transformer amounts to 1 A with rated load and therefore lies within the setting range from 0.3 to 3 A of the used current measuring module.
- The setting current  $I_e$  in the 3RB22, 3RB23 or 3RB24 solid-state overload relay amounts to 1 A.

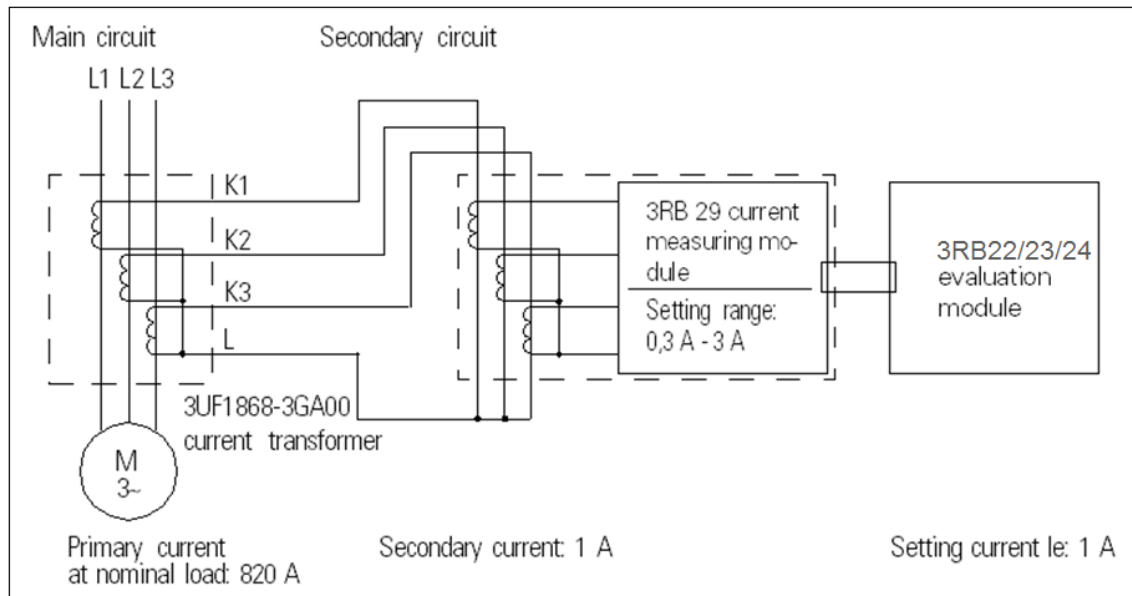


Fig. 2: Example of current measuring with external 3UF1868-3GA00 current transformer (intermediate transformer)


**Note:**

For usage in applications of explosion-proof motors, please contact the technical assistance.

## Overload relays 3RB24 with analog value transmission

The transmission ratio must be taken into account at the overload relay 3 RB24 in the transferred analogue values (current values, rated operational current).

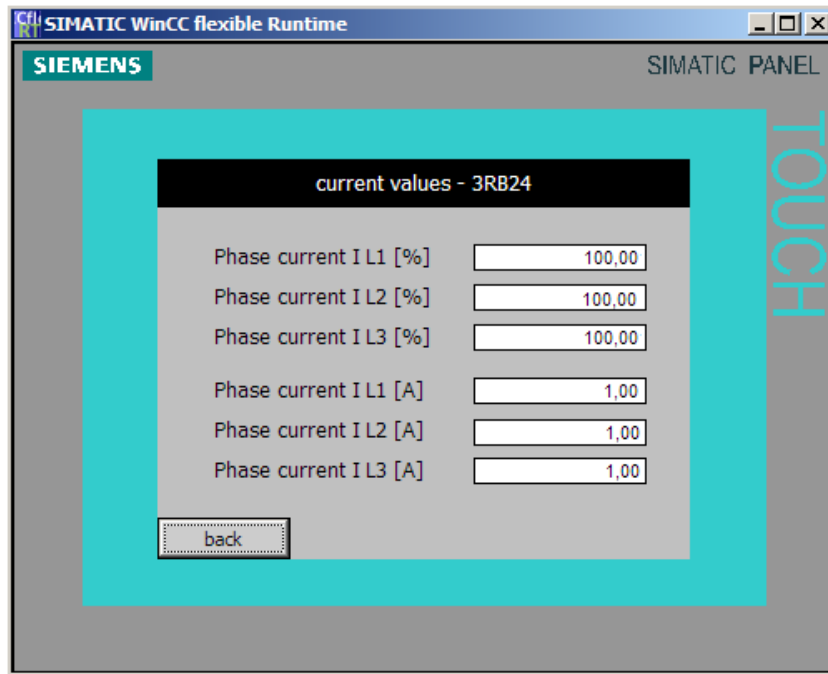Example: With a transmission ratio of 820 the shown/transmitted value of 1 A represents a value of 820 A.



Example in WinCC flexible 2008