

# Industrial Controls SIRIUS Controls

## Contactor Overvoltage Damping

Functional Example No. CD-FE-III-003-V20-EN



# sirius



# SIEMENS

## Comments

Sirius Functional Examples are functional, tested automation configurations based on A&D standard products intended for simple, quick and economic implementation of automation tasks in low-voltage controls. Each of these Functional Examples covers a frequently occurring subtask of a typical customer problem within low-voltage controls.

- 1 Introduction ..... 3**
- 2 Overvoltage Development ..... 4**
- 3 Types of Protective Circuits ..... 5**
  - 3.1 Circuit with RC Elements ..... 5**
  - 3.2 Diode Circuit ..... 6**
    - 3.2.1 Freewheeling Diode Circuit ..... 6
    - 3.2.2 Circuit with One Diode / Zener Diode Diode Assembly ..... 7
  - 3.3 Varistor Circuit ..... 8**
  - 3.4 Overview of Circuit Types ..... 9**
- 4 Siemens – Overvoltage Damping Solutions ..... 9**
  - 4.1 Surge Suppressors for Contactors size S00 and S0 ..... 10**
  - 4.2 Surge Suppressors for Contactors Size S2 to S12 ..... 11**
- 5 Contact Partner ..... 12**
- 6 Guarantee, Liability and Support ..... 12**
- 7 Bibliography ..... 12**

## 1 Introduction

The most significant causes of overvoltage are switching operations in inductive circuits, e.g. contactor coils.

These overvoltages, voltage peaks up to 4 kV, can rapidly attain high values. The consequences include:

- Extreme contact erosion and, thus, premature wear of the contacts that switch the coil.
- Interference signals may be coupled, which, in some cases, could lead to fault signals in electronic controls and destruction of electronic modules.


Therefore, the switching overvoltages of the contactor coils are usually damped with a protective circuit.

The aim of this scientific paper is to provide users with a selection and dimensioning aid, and to list the advantages and disadvantages of the different types of protective circuits.

## 2 Overvoltage Development

Overvoltage develops when the contactor coil is switched off because the coil inductance attempts to continue the current flow during switch-off, whereupon the circuit closes via the self-capacitance of the magnetic coil. If the circuit has sufficient electric strength, current and voltage could flow in the form of a damped oscillation.

Due to the dynamic resistance of the switched-off coil, the oscillation amplitudes are in the range of up to several kV and the voltage rises are in the region of  $1\text{ kV}/\mu\text{s}$ .

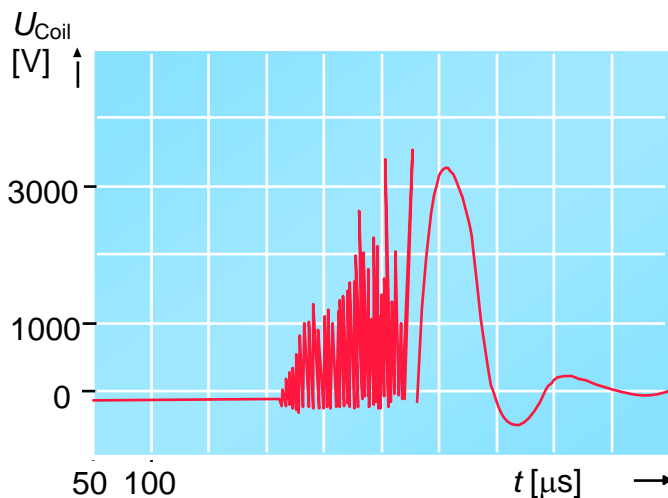

**Fig. 1:** Switching overvoltage of an unconnected contactor relay magnetic coil  
230 V, 50 Hz, 10 VA

Fig. 1 shows the oscillogram of the power down cycle of a contactor relay magnetic coil causing a “shower discharge”. After a shower discharge phase of approximately  $250\ \mu\text{s}$ , a damped oscillation with a peak value of approx. 3.5 kV develops. The shower discharges also cause extreme erosion of the mechanical switching contact.

Furthermore, due to the very steep voltage shapes that develop on capacitive routes, considerable interference signals may be coupled in neighboring systems.

These make switching at the point of origin of the source of interference (i.e. the contactor coil) necessary. In this manner, overvoltage can be prevented directly at the source, thus protecting voltage-sensitive electronic components. The capacitive coupling of interference signals in the control wires of electronic circuitry is also avoided.


Overvoltage damping usually requires the following circuit components, which are switched parallel to the contactor coil:

- RC element (resistance and capacitor in series)
- Freewheeling diode, diode assembly
- Varistors

## 3 Types of Protective Circuits

### 3.1 Circuit with RC Elements

RC elements are used primarily for AC-operated contactors, however, they may also be used for DC-operated contactors.

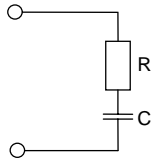


**Fig. 2:** Basic circuit diagram: RC element

The increase in the capacity at the coil reduces the amplitude to 2 to 3 times the control voltage and also reduces the steepness of the switching overvoltage, preventing further shower discharges. The voltage oscillates temporarily to 400 V before gradually running out. Thus, the RC circuit protects  $dv/dt$  sensitive output stages against unwanted through switching.

Correctly selected RC elements hardly influence the switching times of the contactors with a turn-off delay of less than 1 ms. However, optimum damping requires adaptation to the respective rated control voltage and rated frequency. Therefore, the RC elements must be selected according to the catalog.

In Figure 3, the voltage curve with the connected contactor relay magnetic coil from Fig. 1 is depicted with the appropriate RC element.

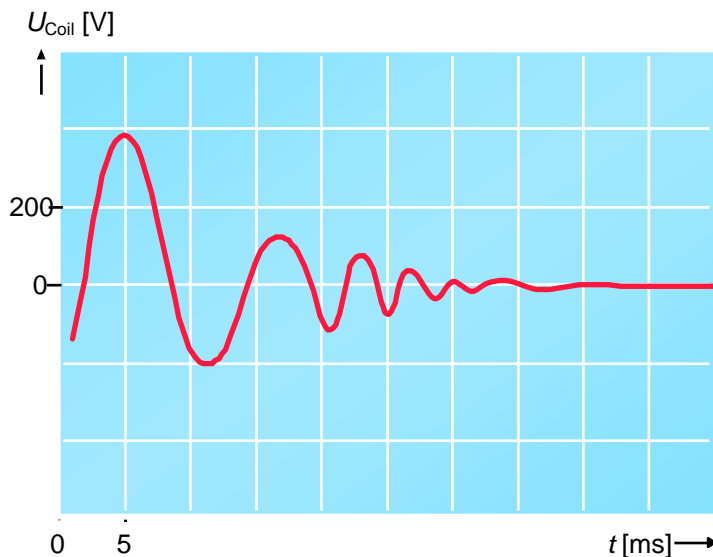

**Fig. 3:** Switching overvoltage of a contactor relay magnetic coil 230 V, 50 Hz, 10 VA for an RC element circuit with 110  $\Omega$ , 0.22  $\mu\text{F}$


## 3.2 Diode Circuit

Switch-off overvoltages can only be avoided when a diode circuit is used in the case of DC-operated contactors. Correct polarity must be ensured when connecting.

### 3.2.1 Freewheeling Diode Circuit


Switching overvoltages do not occur when a diode circuit is implemented; the diode limits to 0.7 V.

However, diodes cause an increase in the breaking delay, breaking time, by a factor of 6 to 9. This characteristic can be used to your advantage if, for example, a temporary voltage drop of around several milliseconds has to be bridged. In the case of contactors larger than size 0/S0, over 5.5 kW, freewheeling diodes can cause a two-stage switching off of the magnet system, which – in a worse case scenario – may cause contact welding. Therefore, freewheeling diodes are no longer recommended in this case.

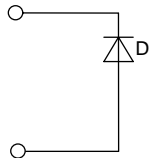

**Fig. 4:** Basic circuit diagram: freewheeling diode

In Figure 5, the voltage curve with the connected contactor relay magnetic coil from Fig. 1 is depicted with the appropriate freewheeling diode.

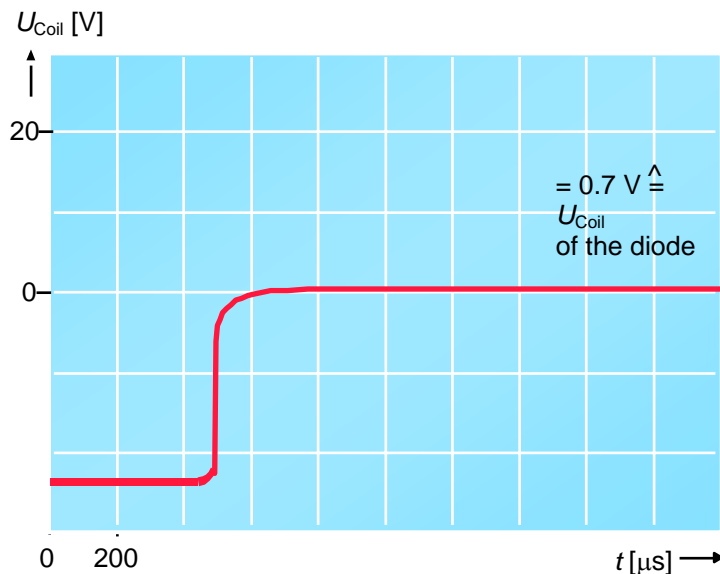


**Fig. 5:** Switching overvoltage of a contactor relay magnetic coil 24 V DC, 3 W for a freewheeling diode circuit

### 3.2.2 Circuit with One Diode / Zener Diode Diode Assembly


Switching overvoltages also do not develop in the case of a contactor coil circuit using a diode assembly consisting of a diode and a Zener diode, since the diode assembly limits the voltage to 10 V.

However, diode assemblies cause an increase in the breaking delay, the break time, by a factor of 2 to 6.

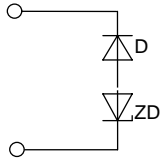

**Fig. 6:** Basic circuit diagram: diode assembly


In Figure 7, the voltage curve with the connected contactor relay magnetic coil from Fig. 1 is depicted with the appropriate diode assembly.

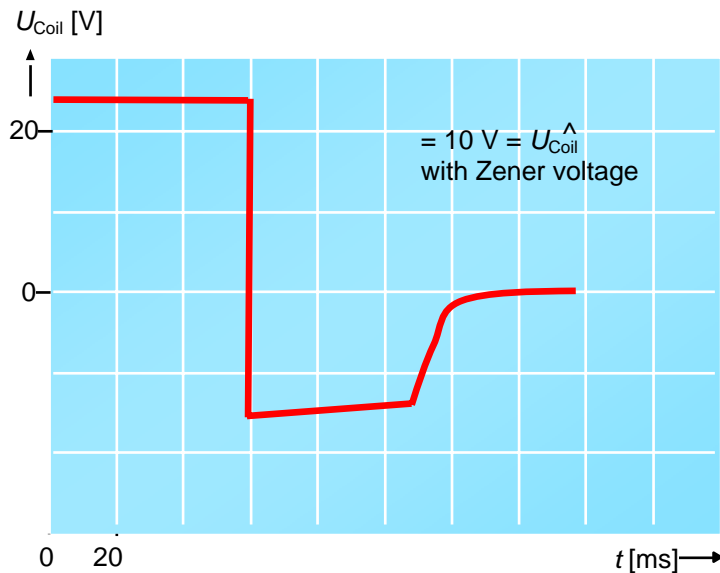

**Fig. 7:** Switching overvoltage of a contactor relay magnetic coil 24 V DC, 3 W with a diode assembly circuit


### 3.3 Varistor Circuit

When wired parallel to a coil, Varistors, voltage-dependent resistors, limit the maximum overvoltage, since they become conductive when a specific threshold voltage is exceeded. Until this point is reached, shower discharges also develop which are similar to those that develop when the magnetic coil is not connected. However, they are of a shorter duration. In contrast to the RC element, they do not reduce the steepness of the voltage rise. They are suitable for DC and AC-operated contactors and have little influence on switching times.

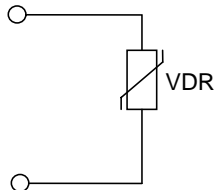

**Fig. 8:** Basic circuit diagram: varistor

In Figure 9, the voltage curve with the connected contactor relay magnetic coil from Fig. 1 is depicted with the appropriate varistor.

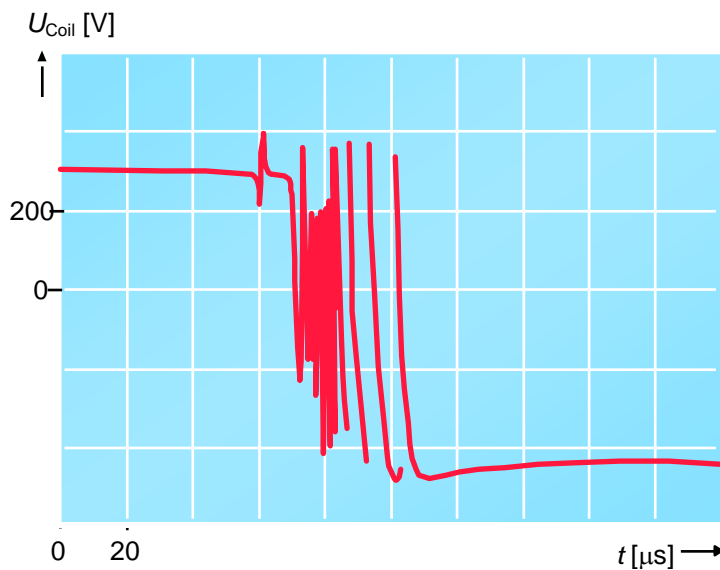

**Fig. 9:** Switching overvoltage of a contactor relay magnetic coil 230 V, 50 Hz, 10 VA  
With a 275-V varistor circuit (initial range: The voltage reduces to zero after approx. 3 ms)



## 3.4 Overview of Circuit Types

Load circuitry	Control supply voltage	Additional dropout delay	Defined induction voltage limiting	Advantages / Disadvantages	Preferred use
Diode	DC	Long	Yes ( $U_D$ )	Advantages: <ul style="list-style-type: none"> <li>• Easily implemented</li> <li>• Reliable</li> <li>• Dimensioning uncritical</li> <li>• Small induction voltage</li> </ul> Disadvantages: <ul style="list-style-type: none"> <li>• Long dropout delay</li> <li>• Only suitable for sizes 00 / S00</li> </ul>	Unstable control commands/ control supply voltage
Diode assembly	DC	Medium	Yes ( $U_{ZD}$ )	Advantages: <ul style="list-style-type: none"> <li>• Dimensioning uncritical</li> </ul> Disadvantages: <ul style="list-style-type: none"> <li>• Damping only above <math>U_{ZD}</math> (10 V)</li> </ul>	In vicinity of EMC-critical components
Varistor	AC / DC	Short 2 – 5 ms	Yes ( $U_{VDR}$ )	Advantages: <ul style="list-style-type: none"> <li>• Energy absorption</li> <li>• Dimensioning uncritical</li> <li>• Easily implemented</li> </ul> Disadvantages: <ul style="list-style-type: none"> <li>• Damping only above <math>U_{VDR}</math></li> </ul>	Suitable for most standard applications, e.g. in SIMATIC environments
RC element	AC / DC	Very short 1 ms	No	Advantages: <ul style="list-style-type: none"> <li>• HF damping thanks to energy storage</li> <li>• Very suitable for AC voltage</li> <li>• Level-independent damping</li> </ul> Disadvantages: <ul style="list-style-type: none"> <li>• High inrush current</li> <li>• Sensitive to harmonics</li> </ul>	For critical switching times

## 4 Siemens – Overvoltage Damping Solutions

The following surge suppressors are available for 3RT1 contactors:

Surge suppressor	With LED	Without LED			
	for S00	for S00	for S0	for S2, S3	for S6 to S12
Noise suppression diode	X	X	--	--	--
Diode assembly	--	X	X	X	--
Varistor	X	X	X	X	Integrated
RC element	--	X	X	X	X

## 4.1 Surge Suppressors for Contactors size S00 and S0

For contactors	Version	Rated control supply voltage $U_s^{1)}$		DT	Order No. <sup>2)</sup>	Price per PU	PU (UNIT, SET, M)
		AC operation	DC operation				
Type		V AC	V DC				

### Surge suppressors without LED (also for Cage Clamp terminals)

#### Size S00



3RT19 16-1DG00

For plugging onto the front side of the contactors with and without auxiliary switch blocks

For contactors	Version	Rated control supply voltage $U_s^{1)}$	Power consumption of LEDs at $U_s$	DT	Order No. <sup>2)</sup>	Price per PU	PU (UNIT, SET, M)
3RT1., 3RH1	<b>Varistors</b>	24 ... 48	24 ... 70	▶	3RT19 16-1BB00		
		48 ... 127	70 ... 150	▶	3RT19 16-1BC00		
		127 ... 240	150 ... 250	A	3RT19 16-1BD00		
		240 ... 400	--	▶	3RT19 16-1BE00		
		400 ... 600	--	A	3RT19 16-1BF00		
3RT1., 3RH1	<b>RC elements</b>	24 ... 48	24 ... 70	▶	3RT19 16-1CB00		
		48 ... 127	70 ... 150	▶	3RT19 16-1CC00		
		127 ... 240	150 ... 250	▶	3RT19 16-1CD00		
		240 ... 400	--	▶	3RT19 16-1CE00		
		400 ... 600	--	▶	3RT19 16-1CF00		
3RT1., 3RH1	<b>Noise suppression diodes</b>	--	12 ... 250	▶	3RT19 16-1DG00		
3RT1., 3RH1	<b>Diode assembly (diode and Zener diode) for DC operation</b>	--	12 ... 250	▶	3RT19 16-1EH00		

#### Size S0



3RT19 26-1B0.00

For fitting onto the coil terminals at top or bottom

For contactors	Version	Rated control supply voltage $U_s^{1)}$	Power consumption of LEDs at $U_s$	DT	Order No. <sup>2)</sup>	Price per PU	PU (UNIT, SET, M)
3RT1. 2	<b>Varistors</b>	24 ... 48	24 ... 70	▶	3RT19 26-1BB00		
		48 ... 127	70 ... 150	▶	3RT19 26-1BC00		
		127 ... 240	150 ... 250	▶	3RT19 26-1BD00		
		240 ... 400	--	▶	3RT19 26-1BE00		
		400 ... 600	--	B	3RT19 26-1BF00		
3RT1. 2	<b>RC elements</b>	24 ... 48	24 ... 70	▶	3RT19 26-1CB00		
		48 ... 127	70 ... 150	▶	3RT19 26-1CC00		
		127 ... 240	150 ... 250	▶	3RT19 26-1CD00		
		240 ... 400	--	▶	3RT19 26-1CE00		
		400 ... 600	--	B	3RT19 26-1CF00		
3RT1. 2	<b>Diode assembly For DC operation</b>						
	• Connectable at the top (e.g. for contactor with overload relay)	--	24	▶	3RT19 26-1ER00		
		--	30 ... 250	▶	3RT19 26-1ES00		
	• Connectable at the bottom (e.g. for fuseless load feeders)	--	24	▶	3RT19 26-1TR00		
		--	30 ... 250	A	3RT19 26-1TS00		

- 1) Can be used for AC operation for 50/60 Hz. Please inquire about further voltages.
- 2) For packs of 10 units, the Order No. must be supplemented with "Z" and the order code "X90".

For contactors	Version	Rated control supply voltage $U_s^{1)}$		Power consumption of LEDs at $U_s$	DT	Order No. <sup>2)</sup>	Price per PU	PU (UNIT, SET, M)
		AC operation	DC operation					
Type		V AC	V DC					

### Surge suppressors with LED (also for Cage Clamp terminals)

#### Size S00







3RT19 16-1L00

For plugging onto the front side of the contactors with and without auxiliary switch blocks

For contactors	Version	Rated control supply voltage $U_s^{1)}$	Power consumption of LEDs at $U_s$	DT	Order No. <sup>2)</sup>	Price per PU	PU (UNIT, SET, M)
3RT1., 3RH1.	<b>Varistors</b>	24 ... 48	12 ... 24	10 ... 120	▶	3RT19 16-1JJ00	
		48 ... 127	24 ... 70	20 ... 470	▶	3RT19 16-1JK00	
		127 ... 240	70 ... 150	50 ... 700	▶	3RT19 16-1JL00	
		--	150 ... 250	160 ... 950	A	3RT19 16-1JP00	
3RT1., 3RH1.	<b>Noise suppression diodes</b>	--	24 ... 70	20 ... 470	▶	3RT19 16-1LM00	
		--	50 ... 150	50 ... 700	▶	3RT19 16-1LN00	
		--	150 ... 250	160 ... 950	▶	3RT19 16-1LP00	

- 1) Can be used for AC operation for 50/60 Hz. Please inquire about further voltages.
- 2) For packs of 10 or 5 units, the Order No. must be supplemented with "Z" and the order code "X90".

## 4.2 Surge Suppressors for Contactors Size S2 to S12

For contactors	Version	Rated control supply voltage $U_s$ <sup>1)</sup>		DT	Order No. <sup>2)</sup>		
		AC operation	DC operation				
Type		V AC	V DC				
<b>Surge suppressors without LED (also for Cage Clamp terminals)</b>							
<i>Sizes S2 and S3</i>							
<b>For fitting onto the coil terminals at top or bottom</b>							
 3RT19 26-1B0.00	3RT1. 3, 3RT1. 4	<b>Varistors</b>		24 ... 48	24 ... 70	▶	3RT19 26-1BB00
		48 ... 127	70 ... 150	▶	3RT19 26-1BC00		
		127 ... 240	150 ... 250	▶	3RT19 26-1BD00		
		240 ... 400	–	▶	3RT19 26-1BE00		
		400 ... 600	–	B	3RT19 26-1BF00		
 3RT19 36-1C.00	3RT1. 3 <sup>3)</sup> , 3RT1. 4	<b>RC elements</b>		24 ... 48	24 ... 70	▶	3RT19 36-1CB00
		48 ... 127	70 ... 150	▶	3RT19 36-1CC00		
		127 ... 240	150 ... 250	▶	3RT19 36-1CD00		
		240 ... 400	–	▶	3RT19 36-1CE00		
		400 ... 600	–	B	3RT19 36-1CF00		
 3RT19 36-1E00	3RT1. 3, 3RT1. 4	<b>Diode assembly</b>					
		For DC operation					
		• Connectable at the top (e.g. for contactor with overload relay)		24	▶	3RT19 36-1ER00	
				30 ... 250	▶	3RT19 36-1ES00	
		• Connectable at the bottom (e.g. for fuseless load feeders)		24	▶	3RT19 36-1TR00	
		30 ... 250	B	3RT19 36-1TS00			
<i>Sizes S6 ... S12</i>							
<b>For connecting to withdrawable coil with screw terminals with contactors with</b>							
• 3RT1. ...A... conventional operating mechanism							
• 3RT1. ...N... solid-state operating mechanism							
 3RT19 56-1C.00	3RT1. 5, 3RT1. 6, 3RT1. 7	<b>RC elements</b>		24 ... 48	24 ... 70	▶	3RT19 56-1CB00
		48 ... 127	70 ... 150	▶	3RT19 56-1CC00		
		127 ... 240	150 ... 250	▶	3RT19 56-1CD00		
		240 ... 400	–	▶	3RT19 56-1CE00		
		400 ... 600	–	C	3RT19 56-1CF00		

1) Can be used for AC operation for 50/60 Hz. Please inquire about further voltages.

3) Mountable only at the top for 3RT1. 3/AC operating mechanism

2) For packs of 10 or 5 units, the Order No. must be supplemented with 'Z' and the order code 'X90'.

## 5 Contact Partner

### Technical Assistance for Low-voltage Controls and Distribution

Personally from Mon. – Fri. 8:00 am to 5:00 pm (CET)

Telephone: +49 (911)-895-5900

E-mail: Internet: By fax, around the clock

Fax: +49 (911)-895-5907

## 6 Guarantee, Liability and Support

We are not liable for any of the information contained in this document.

We are not liable for any damage caused by use of the examples, advice, programs, configuration and performance data, etc. described in this Sirius Function Example, independent of the legal ground this is based upon, unless we are imperatively liable according to the product liability law due to, e.g., cases of premeditation, an act of gross negligence, injury to life, body or health, or unless the quality of a product has been guaranteed, or due to fraudulent concealment of a defect or serious breach of contract. Damages due to serious breach of contract are, however, restricted to prevalent and predictive contractual damages, in as much as premeditation or gross negligence are not existent or there is no imperative liability due to injury to life, body or health. This does not constitute a change in the burden of proof to your disadvantage.

## 7 Bibliography

- [1] Schalten, Schützen, Verteilen in Niederspannungsnetzen, Fachbuch Siemens [Switching, Protection and Distribution in Low-Voltage Networks” (Siemens reference book)]

Copyright© 2006 Siemens A&D.

Propagation or reproduction of these Safety Function Examples or parts thereof is not permitted unless expressly allowed by Siemens A&D.